

# Counters and Registers

## 1. Concept of Registers

A

is a small, fast storage unit in a digital system made up of a group of connected together. It is used to store multiple bits of binary data temporarily during processing operations.

Since each flip-flop can store :

- A contains

and can store 4 bits of data

- An contains and can store 8 bits of data

Registers are very important because they provide quick access to data during system operations.

**Main Functions  
of Registers**

✓

**Registers hold data while it is being processed by the CPU.**

✓

**They move data between different parts of a digital system.**

✓

**Some registers support shifting and arithmetic operations.**

## **Areas Where Registers Are Used**

- In the , such as the accumulator, instruction register, and data register
- In for buffering data
- In to handle serial and parallel data

## 2. Types of Registers

Registers are classified based on how data enters and leaves them.

### (a) SISO – Serial In Serial Out

In a , data enters and also leaves in the same sequence.

✓ Input is serial

✓

Output is serial

This type of register is mainly used in:

- Data transmission systems

- Delay circuits

**(b) SIPO –**  
**Serial In Parallel Out**

In a , data enters serially but is available at the output in .

✓ **Input: one bit at a time**

✓

**Output: all bits at once**

**This is useful when:**

- **Converting serial data to parallel data**
- **Receiving data from communication channels**

**(c) PISO –  
Parallel In Serial Out**

In a , multiple bits are loaded at the same time (parallel) and then shifted out one by one (serially).

✓ Input: parallel

✓

Output: serial

Used in:

- Data transmission
- Reducing number of wires required

**(d) PIPO –  
Parallel In Parallel Out**

In a , data is loaded and taken out simultaneously in parallel form.

✓ Input: parallel

✓

Output: parallel

This type is best for:

- High-speed data storage
- Temporary data holding inside processors

### 3. Shift Registers

A is a register that shifts its stored data either when a clock pulse is applied.

Each clock pulse moves the data by one position.

## Types of Shift Registers

- – shifts data towards left

- – shifts data towards right

- – can shift in both directions

## Applications of Shift Registers

- ✓ Moving data between registers

- ✓ Performing arithmetic shifts (multiplication/division by 2)

- ✓ Temporary data storage

- ✓ Used in communication systems such as serial data transmission

## 4.

### **Applications of Registers**

**Registers play many roles in digital systems:**

- **Storing instructions in the CPU**
- **Holding data for processing**
- **Acting as buffers between system units**
- **Converting data between serial and parallel formats**
- **Speeding up computer operations**

## 5. Counter

### **Basics**

A

is a type of sequential circuit designed to applied to it.  
With every clock pulse, the counter changes  
its state in a predefined binary sequence.

**Example: 3-bit  
Binary Counter**

$000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 110 \rightarrow 111$   
After reaching 111, it resets to 000.

**Common Uses of  
Counters**

✓ Digital clocks

✓  
Timers

✓  
Event counting systems



## Frequency measurement devices

### 6. Ripple vs Synchronous Counters

Counters can be classified based on how clock pulses are applied.

#### Ripple (Asynchronous) Counter

- Clock pulse is applied only to the first flip-flop
- The output of one flip-flop triggers the next
- Each flip-flop changes state after the previous one

⚠ This causes delay known as

✓ Simple design

## ✗ Slower operation

### Synchronous Counter

- All flip-flops receive the clock signal at the same time
- All states change simultaneously

✓ Fast

✓

Accurate

✗ More complex circuit design

## **Comparison Table**

### **Feature**

**Ripple  
Counter**

**Synchronous  
Counter**

**Speed**

**Slow**

**Fast**

**Delay**

**High**

Very  
low

Design

Simple

Complex

## Usage

**Small  
systems**

**Modern  
systems**

**7. Up/Down  
Counters**

**Up Counter**

**Counts forward in increasing order:**

$0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 4 \dots$

## **Down Counter**

**Counts backward:**

$4 \rightarrow 3 \rightarrow 2 \rightarrow 1 \rightarrow 0 \dots$

## **Up/Down Counter**

**Has a control input that determines counting direction.**

**✓ If control = 1  $\rightarrow$  counts up**

**✓**

**If control = 0  $\rightarrow$  counts down**

## Applications

- Elevator control systems
- Digital scoreboards
- Timers and clocks

### 8. Mod-N

#### Counters

A is a counter that counts from and then resets back to zero.

Example:

Mod-10 Counter

Counts:

0 → 1 → 2 → 3 → 4 → 5 → 6 → 7 → 8 → 9 → reset

## Where Mod-N Counters Are Used

✓ Digital clocks (seconds, minutes)

✓  
Calculators

✓  
Frequency dividers

✓  
Electronic displays

## 9. Mod-10 Counter Design (Simple Explanation)

To design a :

Step 1:  
Determine number of flip-flops

Since:

$2^3 = 8$  (not enough)

$2^4 = 16$  (sufficient)

👉 Use

Step 2: Normal  
Counting

The counter counts naturally:

0000 (0)  $\rightarrow$  0001 (1)  $\rightarrow$  ...  $\rightarrow$  1001 (9)

Step 3: Reset  
Condition

**When the counter reaches:**

**1010 (10)**

**A logic gate detects this and sends a to bring it back to:**

**0000 (0)**

**This ensures the counter only counts from 0 to**

**9.**

## **CONCLUSION**

**Registers and counters are fundamental  
building blocks of digital systems.**

- Registers store and transfer binary data**
- Shift registers move data efficiently**

- Counters track events and time
- Mod-N counters control counting limits

Together, they form the backbone of computers, digital clocks, and control systems.